

Chapter 16: Capacitors


Practical Application Worksheet

Instructions: Circle the correct answer for each multiple-choice question. Use the blank space provided below each question to show your calculation steps.

1. What are the two parallel conducting plates of a capacitor commonly called, and what type of material separates them?
 - A. Armatures (conductors) separated by a dielectric (insulator).
 - B. Dielectrics (insulators) separated by an armature (conductor).
 - C. Terminals (insulators) separated by a vacuum.
 - D. Armatures (insulators) separated by a dielectric (conductor).
2. A capacitor has a capacitance of $5\ \mu\text{F}$ and is connected to a $12\ \text{V}$ battery. What is the total charge stored on its positive plate?
 - A. $2.4\ \mu\text{C}$
 - B. $17\ \mu\text{C}$
 - C. $60\ \mu\text{C}$
 - D. $600\ \mu\text{C}$
3. How much electrostatic energy is stored in a $10\ \mu\text{F}$ capacitor that is fully charged to $20\ \text{V}$?
 - A. $100\ \mu\text{J}$
 - B. $200\ \mu\text{J}$
 - C. $2\ \text{mJ}$
 - D. $4\ \text{mJ}$
4. A parallel-plate air capacitor has square plates of side length $10\ \text{cm}$ and a separation distance of $2\ \text{mm}$. Given the permittivity of free space $\epsilon_0 \approx 8.85 \times 10^{-12}\ \text{F/m}$, what is its approximate capacitance C_0 ? (Note: $\epsilon_r = 1$ for air).
 - A. $8.85\ \text{pF}$
 - B. $22.1\ \text{pF}$
 - C. $44.25\ \text{pF}$
 - D. $4.42\ \text{nF}$

5. A parallel-plate air capacitor has a capacitance of C_0 . If the air is replaced entirely by mica, which has a relative permittivity of $\epsilon_r = 5.4$, what is the new capacitance?
- A. $C_0/5.4$
 - B. $C_0 - 5.4$
 - C. $C_0 + 5.4$
 - D. $5.4C_0$
6. Two capacitors, $C_1 = 4\ \mu F$ and $C_2 = 12\ \mu F$, are connected in series. What is the equivalent capacitance of this combination?
- A. $3\ \mu F$
 - B. $8\ \mu F$
 - C. $16\ \mu F$
 - D. $48\ \mu F$
7. A circuit requires an equivalent capacitance of $15\ \mu F$. If you already have a $10\ \mu F$ capacitor installed, what component should you connect in parallel with it to reach the target?
- A. A $2.5\ \mu F$ capacitor
 - B. A $5\ \mu F$ capacitor
 - C. A $30\ \mu F$ capacitor
 - D. A $150\ \mu F$ capacitor
8. An RC circuit is built using a $20\ k\Omega$ resistor and a $50\ \mu F$ capacitor. What is the time constant (τ) of this circuit?
- A. $0.1\ s$
 - B. $1.0\ s$
 - C. $2.5\ s$
 - D. $1000\ s$
9. An completely uncharged capacitor is connected in series with a resistor and a $10\ V$ power supply. What is the approximate voltage across the capacitor at exactly $t = \tau$?
- A. $3.7\ V$
 - B. $5.0\ V$
 - C. $6.3\ V$
 - D. $10.0\ V$

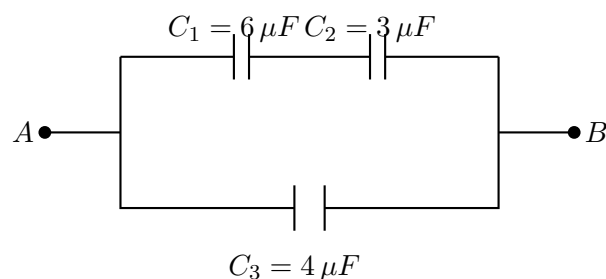10. A capacitor is fully charged to 24 V . The power supply is disconnected, and the capacitor begins to discharge through a resistor. What will be the approximate voltage across the capacitor at $t = \tau$?
- A. 0 V
 B. 8.9 V
 C. 12.0 V
 D. 15.1 V
11. If the distance d between the two plates of a parallel-plate capacitor is halved while keeping the overlapping area constant, how does the capacitance change?
- A. It halves.
 B. It remains unchanged.
 C. It doubles.
 D. It quadruples.
12. A capacitor stores an electrostatic energy W when connected to a potential difference U . If the voltage applied to this exact same capacitor is doubled to $2U$, what is the newly stored energy?
- A. $0.5W$
 B. W
 C. $2W$
 D. $4W$
13. Three capacitors are connected in a complex circuit as shown below. $C_1 = 6\text{ }\mu\text{F}$ and $C_2 = 3\text{ }\mu\text{F}$ are connected in series. This series branch is connected in parallel with a third capacitor, $C_3 = 4\text{ }\mu\text{F}$. What is the total equivalent capacitance (C_{eq}) between points A and B?



- A. $1.33\text{ }\mu\text{F}$
 B. $2.4\text{ }\mu\text{F}$
 C. $6.0\text{ }\mu\text{F}$

D. $13.0\,\mu F$

14. Refer to the circuit diagram from the previous question. If a constant DC voltage of $U_{AB} = 12\,V$ is applied across the entire combination, determine the charge Q_1 , the voltage U_1 , and the stored electrostatic energy W_1 of capacitor C_1 .

- A. $Q_1 = 24\,\mu C$, $U_1 = 4\,V$, $W_1 = 48\,\mu J$
- B. $Q_1 = 72\,\mu C$, $U_1 = 12\,V$, $W_1 = 432\,\mu J$
- C. $Q_1 = 24\,\mu C$, $U_1 = 8\,V$, $W_1 = 96\,\mu J$
- D. $Q_1 = 48\,\mu C$, $U_1 = 4\,V$, $W_1 = 24\,\mu J$